


EEE101

Assignment 1a

Name: Souvik Barman Ratul

ID : 24121205

Ans to the Q. No-1

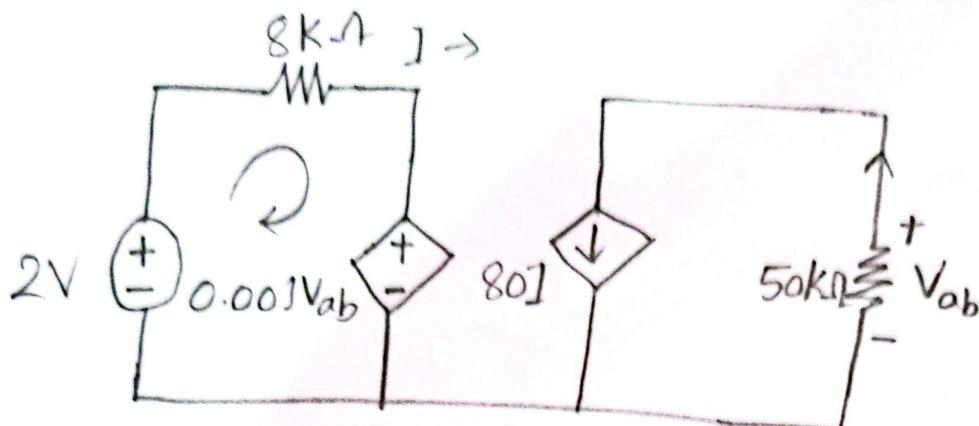

Applying KVL law,

$$-2 + 8000I + 0.001 V_{ab} = 0 \dots \textcircled{i}$$

Applying ohm's law,

$$\begin{aligned} V_{ab} &= R \cdot I = 50 \times 1000 \times (-80I) \\ &= -4000000I \dots \textcircled{ii} \end{aligned}$$

now, $\textcircled{i} \Rightarrow$

$$\begin{aligned} -2 + 8000I + 0.001(-4000000I) &= 0 \\ \Rightarrow -2 + 8000I - 4000I &= 0 \end{aligned}$$

$$\Rightarrow 4000I = 2$$

$$\therefore I = \frac{1}{2000}$$


$$\textcircled{ii} \Rightarrow V_{ab} = -4000000 \times \frac{1}{2000}$$

$$= -2000V$$

$$= -2 KV$$

Ans

Ans to the Q. No - 2

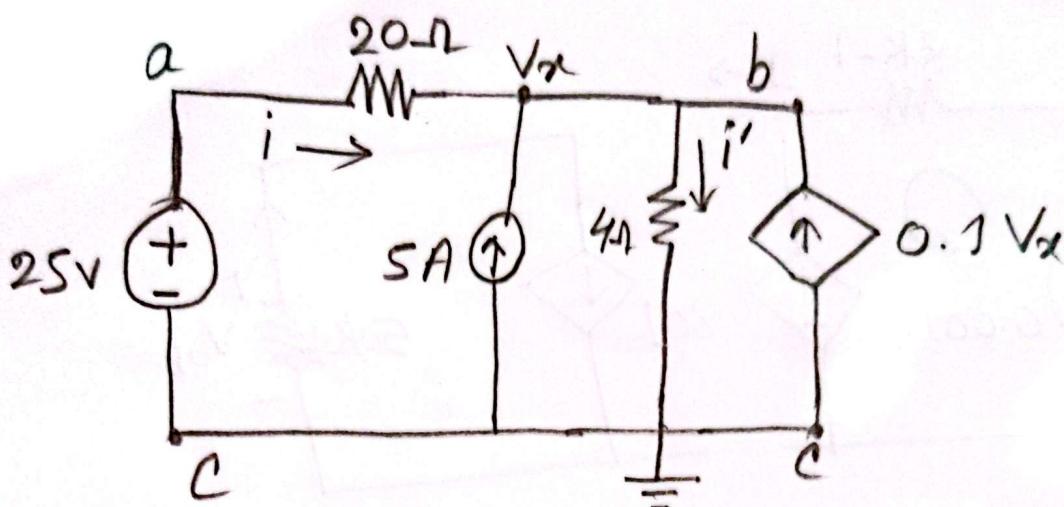

Applying ohm's law,

$$i = \frac{25 - V_x}{20}, \quad i' = \frac{V_x - 0}{4} = \frac{V_x}{4}$$

Applying KCL law, (b node)

$$i + 5 + 0.1 V_x = i' = \frac{V_x}{4} = 1.25 = 1.25$$

$$\Rightarrow \frac{25 - V_x}{20} + 5 + 0.1 V_x = \frac{V_x}{4}$$

$$\Rightarrow \frac{25 - V_x + 100 + 2 V_x}{20} = \frac{V_x}{4}$$

$$\Rightarrow 125 + V_x = 5 V_x$$

$$\Rightarrow 4 V_x = 125$$

$$V_x = 31.25 \text{ V} \quad \underline{\text{Ans}}$$

Ans to the Q.No-5

Given that,

$$q(t) = 100(1 + e^{-2.5t}) \text{ coulombs}$$

$$V(t) = 20e^{1.2t} \text{ V}$$

a) we know,

$$i = \frac{dq}{dt}$$

$$\Rightarrow i = \frac{d}{dt} \{ 100(1 + e^{-2.5t}) \}$$

$$\Rightarrow i = 100 \left\{ \frac{d}{dt}(1) + \frac{d}{dt}(e^{-2.5t}) \right\}$$

$$\Rightarrow i = 100 \left\{ 0 + -2.5e^{-2.5t} \right\}$$

$$\Rightarrow i = -250e^{-2.5t}$$

$$\therefore i(t) = -250e^{-2.5t} \text{ A } \underline{\text{Ans}}$$

b) At $t = 1 \text{ s}$,

$$i = -250 \cdot e^{-2.5(1)} = -20.52 \text{ A}$$

$$V = 20 \cdot e^{1.2(1)} = 66.402 \text{ V}$$

Ans

c) From 'b',

$$i = -20.52 \text{ A}, V = 66.402 \text{ V}$$

The power at $t = 1 \text{ s}$,


$$P = VI$$

$$= (66.402)(-20.52)$$

$$= -1362.569 \text{ W}$$

\therefore The power is negative. So, the device is delivering power at $t = 1 \text{ s}$.

Ans to the Q. No - 6

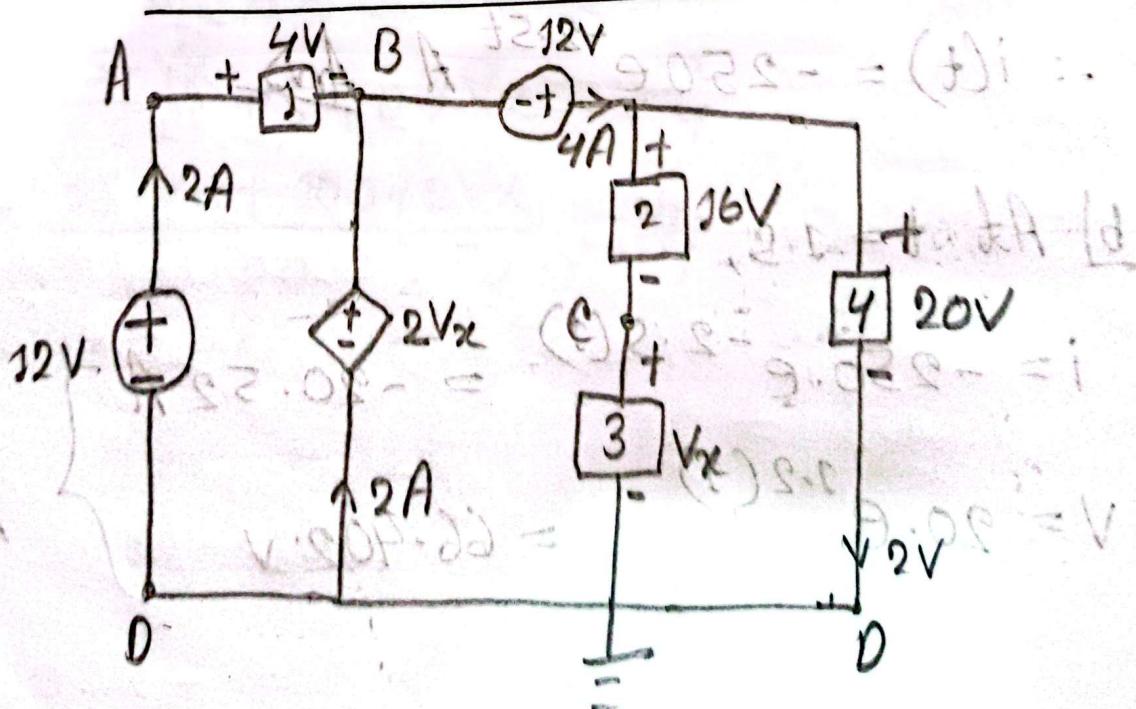

For element 1.

$$V_1 = V_a - V_b$$

$$\Rightarrow 4 = 12 - V_b$$

$$V_b = 12 - 4 = 8 \text{ V}$$

now,

$$2V_x = 8 - 0$$


$$\therefore V_x = 4 \text{ V}$$

For element 3,

$$\begin{aligned} P &= V_x I = (4 \times 2) \text{ W} \\ &= 8 \text{ W}. \end{aligned}$$

The power is positive, so element 3 is absorbing the power. Ans

Ans to the Q. NO-7

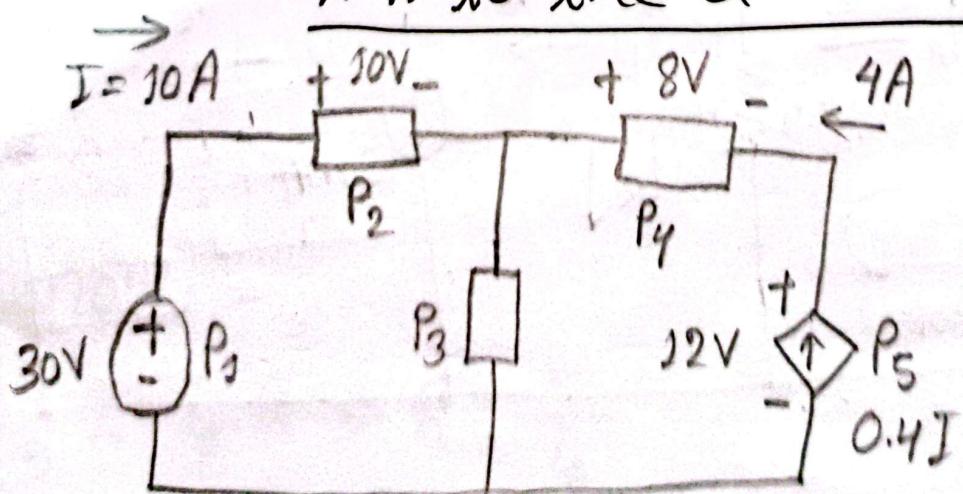

We know that,

$$\sum P = 0$$

$$\Rightarrow P_1 + P_2 + P_3 + P_4 + P_5 = 0$$

$$\Rightarrow (-30 \times 10) + (10 \times 10) + (P_3 - 4 \times 8) - (2 \times 4) = 0$$


$$\Rightarrow -300 + 100 + P_3 - 32 - 48 = 0$$

$$\Rightarrow P_3 - 280 = 0$$

$$\therefore P_3 = 280 \text{ W}$$

The power of P_3 is positive, so the ~~resistor~~ element 3 is absorbing the power.

Ans to the Q. No-3

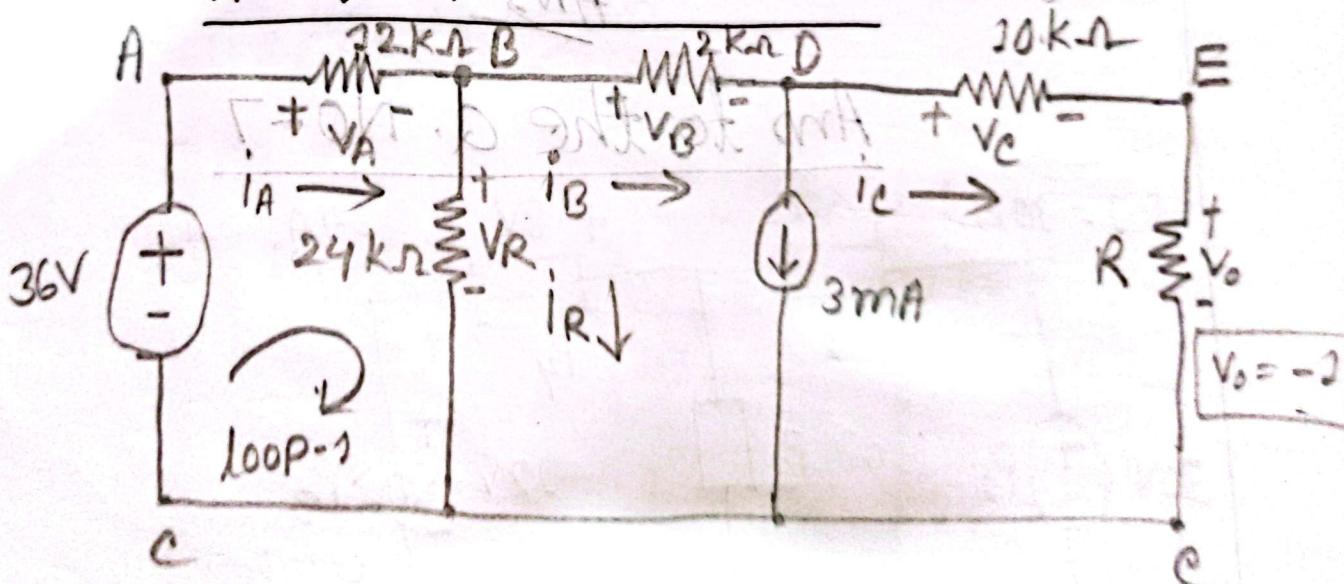

Applying ohm's law,

$$V_A = 12i_A, V_R = 24i_R, V_B = 2i_B, V_C = 10i_C$$

Applying KCL to node B, $i_A = i_B + i_R \dots \textcircled{i}$

Applying KCL to node D, $i_B = 3 + i_C \dots \textcircled{ii}$

Applying KVL to loop-1,

$$-36 + V_A + V_R = 0$$

$$\Rightarrow -36 + 12i_A + 24i_R = 0$$

$$\therefore i_A + 2i_R = 3 \dots \textcircled{iii}$$

Applying KVL to around the loop,

$$-36 + V_A + V_B + V_C + V_o = 0$$

$$\Rightarrow -36 + 12i_A + 2i_B + 10i_C = 0$$

$$\therefore 12i_A + 2i_B + 10i_C = 36 \dots \textcircled{iv}$$

from, $\textcircled{i}, \textcircled{ii}, \textcircled{iii}, \textcircled{iv} \Rightarrow i_A = \frac{17}{6} \text{ mA}, i_B = \frac{11}{4} \text{ mA}$

now,

$$i_C = -\frac{1}{4} \text{ mA}, i_R = \frac{1}{12} \text{ mA}$$

$$V_o = i_C \cdot R \Rightarrow R = \frac{V_o}{i_C} = \frac{-1}{-\frac{1}{4}} = 4 \text{ k}\Omega \quad \underline{\text{And}}$$

Ans to the q. No-4

using wye-Delta trams

$$R_a = \frac{(10 \times 20) + (10 \times 40) + (20 \times 40)}{20} = 70\Omega$$

$$R_b = \frac{(10 \times 20) + (10 \times 40) + (20 \times 40)}{10} = 140\Omega$$

$$R_c = \frac{(10 \times 20) + (10 \times 40) + (20 \times 40)}{40} = 35\Omega$$

$$R_{eq} = 35 \parallel \left\{ (140 \parallel 60) + (70 \parallel 60) \right\}$$




$$= 35 \parallel \frac{427}{6}$$

$$= 23.46\Omega$$

now,


$$I_o = \frac{V_m}{R_{eq}}$$
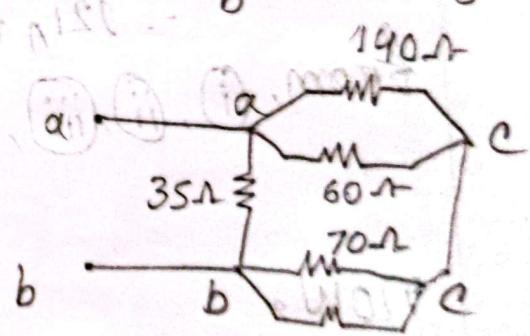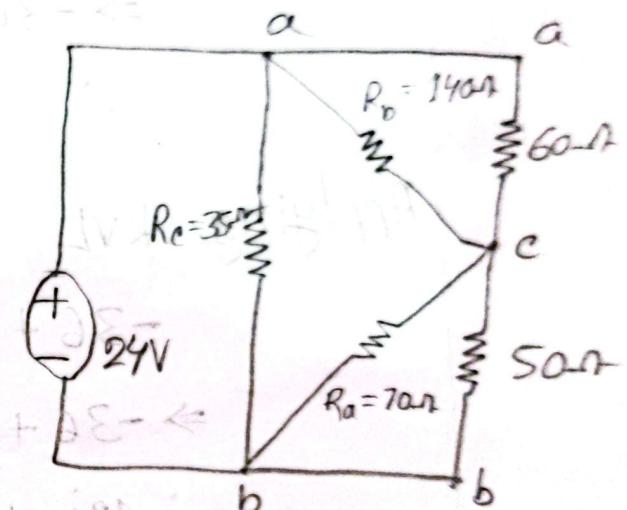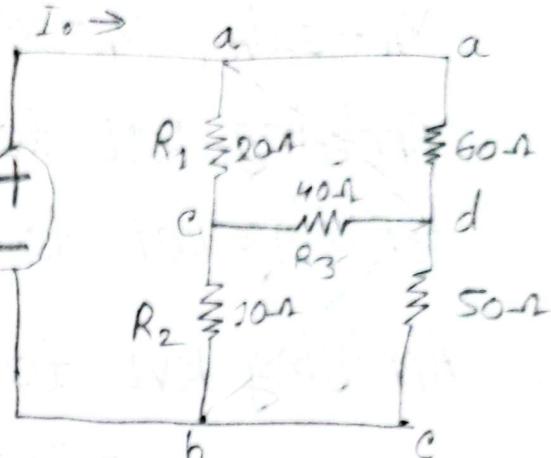
$$= \frac{24}{23.46} = \frac{24}{23.46} = 1.02 \approx 1A$$




Ans to the Q. No - 10

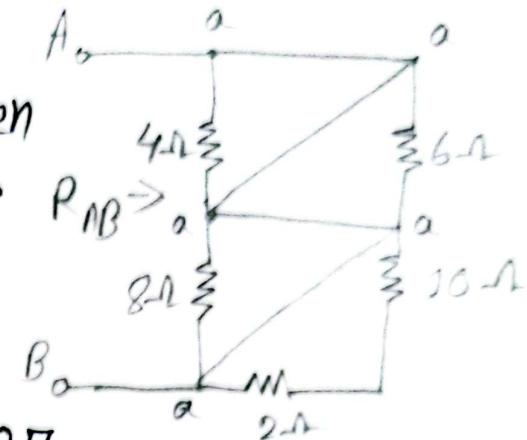a) A resistor works if there is a voltage difference between its two terminals. In here the resistor ends are connected to same node, the voltage difference across the resistor is 0. So, no current flows through any of the resistor. So, R_{AB} at terminal A-B is 0.



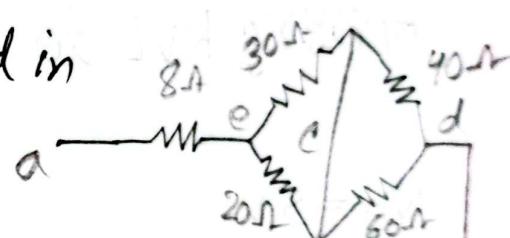
b) 30 ohm and 20 ohm are connected in parallel.

$$\therefore \frac{1}{R_{P_1}} = \frac{1}{30} + \frac{1}{20} \therefore R_{P_1} = 12 \Omega$$



40 ohm and 60 ohm are connected in parallel.
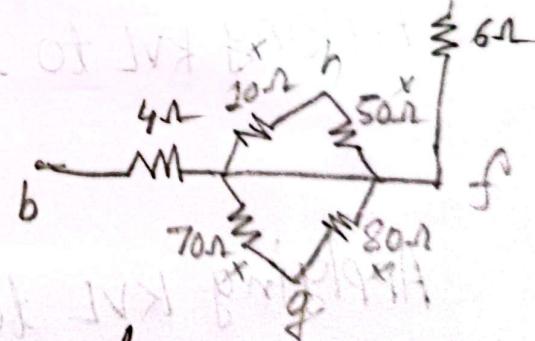
$$\therefore \frac{1}{R_{P_2}} = \frac{1}{40} + \frac{1}{60} \therefore R_{P_2} = 24 \Omega$$




R_{P_1} , R_{P_2} , 8 ohm, 6 ohm, 4 ohm are connected in series.

$$R_s = 8 + 12 + 24 + 6 + 4$$

$$= 54 \Omega$$

Ans

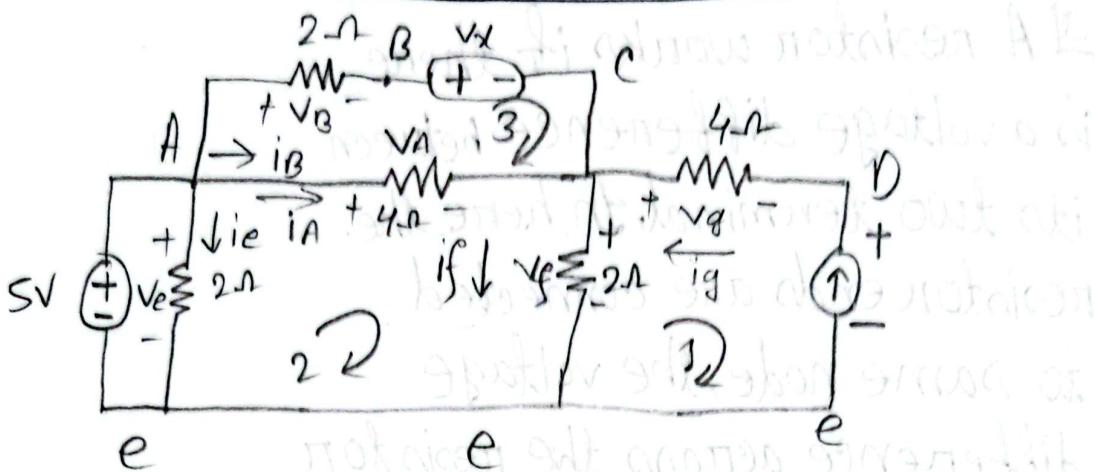Ans to the Q. No - 8

For, 5A Current Source, $V = \frac{50}{5} = 10V$
 $\therefore V_g = -5 \times 4 = -20V$.

Applying KVL to loop 1, $-V_f + V_g + 10 = 0$

$$\Rightarrow V_f = V_g + 10 = -20 + 10 = -10V$$

$$V_e = 5V$$

Applying KVL to loop 2, $-V_e + V_A + V_f = 0$

$$\Rightarrow -5 + V_A - 10 = 0$$

$$\therefore V_A = 15V$$

Applying KVL to loop 3, $V_B + V_X - V_A = 0$

$$\Rightarrow V_B + V_X = V_A$$

$$\Rightarrow V_B + V_X = 15 \dots \textcircled{1}$$


Applying KCL to node C, $i_B + 5 + i_A = i_f$

$$\Rightarrow i_B + 5 + \frac{15}{4} = -\frac{10}{2} \therefore i_B = -5.75A$$

$$\therefore V_B = -13.75 \times 2 = -27.5V$$

$$\therefore V_x = 15 - V_B = 15 + 27.5 = 42.5V \text{ And}$$

Ans to the Q. NO - 9

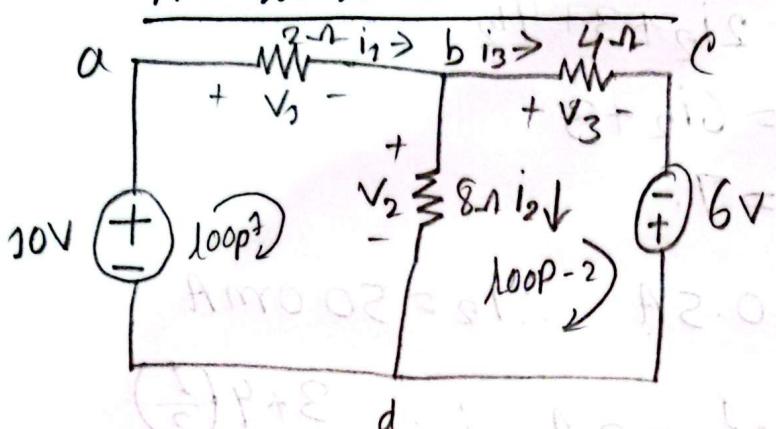

Applying Ohm's law, $V_1 = 2i_1$, $V_2 = 8i_2$, $V_3 = 4i_3$

Applying KCL to node, $i_1 = i_2 + i_3 \dots \textcircled{i}$

Applying KVL to loop-1, $-10 + V_1 + V_2 = 0$

$$\Rightarrow V_1 + V_2 = 10$$

$$\Rightarrow 2i_1 + 8i_2 = 10$$

$$\Rightarrow i_1 + 4i_2 = 5 \dots \textcircled{ii}$$

Applying KVL to loop-2, $V_3 - 6 - V_2 = 0$

$$\Rightarrow V_3 - V_2 = 6$$

$$\Rightarrow 4i_3 - 8i_2 = 6$$

from \textcircled{i}, \textcircled{ii} \Rightarrow

$$\Rightarrow 2i_3 - 4i_2 = 3 \dots \textcircled{iii}$$

$$i_1 = 5 - 4i_2$$

$$i_3 = \frac{3 + 4i_2}{2}$$

(i) \Rightarrow

$$i_1 = i_2 + i_3$$

$$\Rightarrow 5 - 4i_2 = i_2 + \frac{3+4i_2}{2}$$

$$\Rightarrow 10 - 8i_2 = 2i_2 + 3 + 4i_2$$

$$\Rightarrow 10 - 8i_2 = 6i_2 + 3$$

$$\Rightarrow 54i_2 = 7.$$

$$\therefore i_2 = 0.5A \quad \therefore i_2 = 500mA$$

$$\therefore i_1 = 5 - 4 \times \frac{1}{2} = 3A, i_3 = \frac{3+4\left(\frac{1}{2}\right)}{2} = 2.5A.$$

$$\therefore V_1 = 2 \times 3, V_2 = 8 \times \frac{1}{2}, V_3 = 2.5 \times 4 \\ = 6V \quad = 4V \quad = 10V \text{ Ans}$$

(ii)

$$0 = v - 2 - 3v + 8 - 900k \text{ or } 1v = 899k \text{ Ans}$$

$$0 = 5v - 5v \Leftarrow$$

$$0 = 18 - 18 \Leftarrow$$