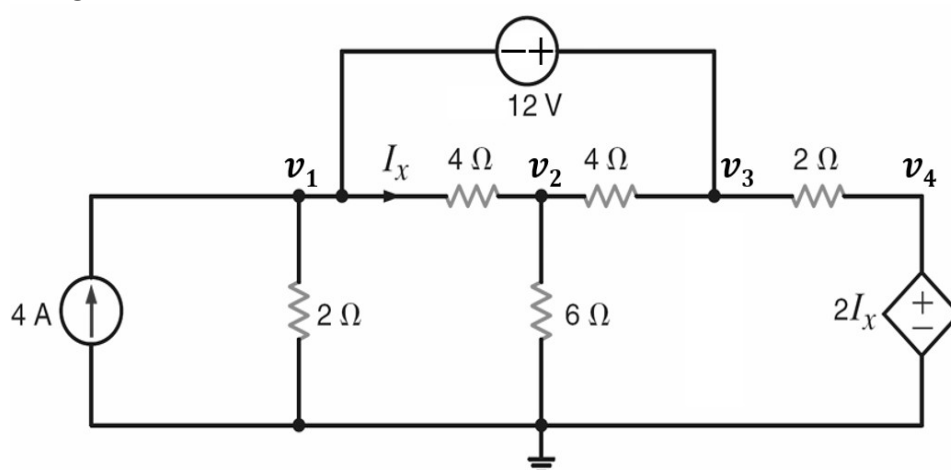


BRAC University
Department of Electrical & Electronic Engineering
Assignment 1b, Spring 2025
EEE/ECE101: Electrical Circuits I

Total Marks: 120


Q1. [10 marks]

Apply the **nodal analysis technique** to find the node voltages, v_1 , v_2 , v_3 , and v_4 in the following circuit.



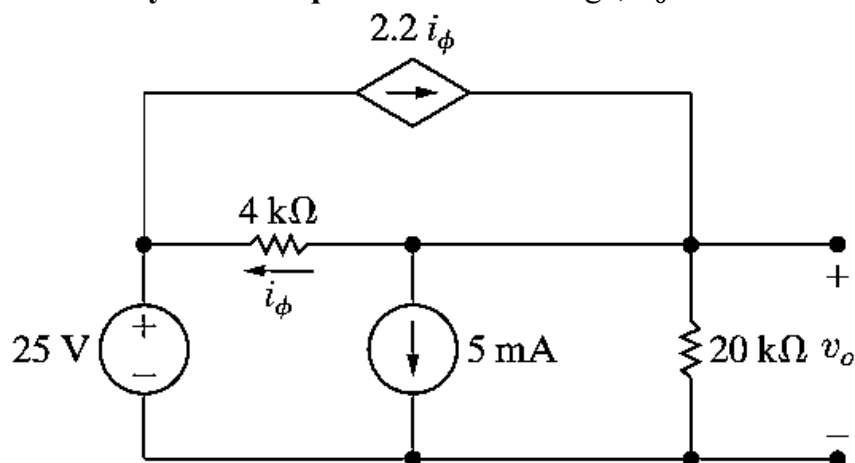
Q2. [10 marks]

Apply the **nodal analysis technique** to find the voltage, v_o in the following circuit.



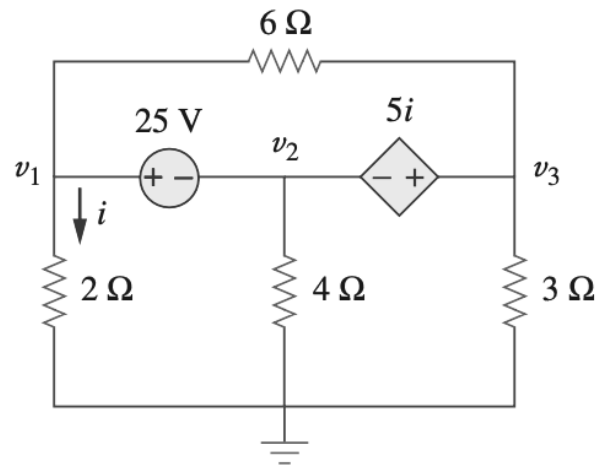
Q3. [10 marks]

Apply the **nodal analysis technique** to find the node voltages, v_1 , v_2 , and v_3 in the following circuit.



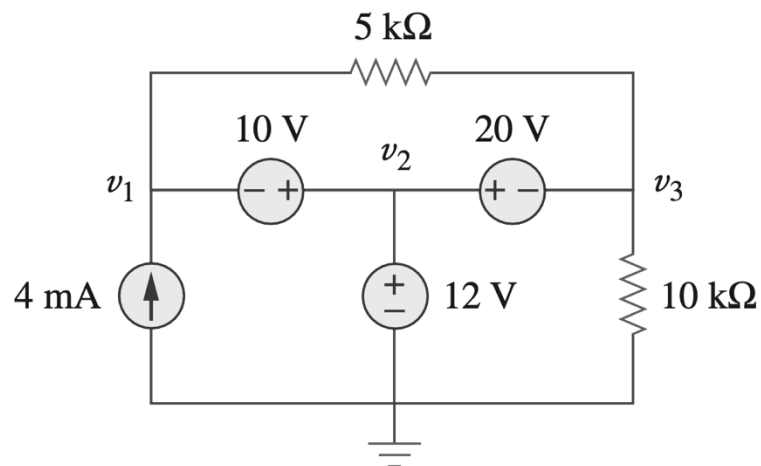
Q4. [10 marks]

Apply the **nodal analysis technique** to find the node voltages, v_1 , v_2 , and v_3 in the following circuit.



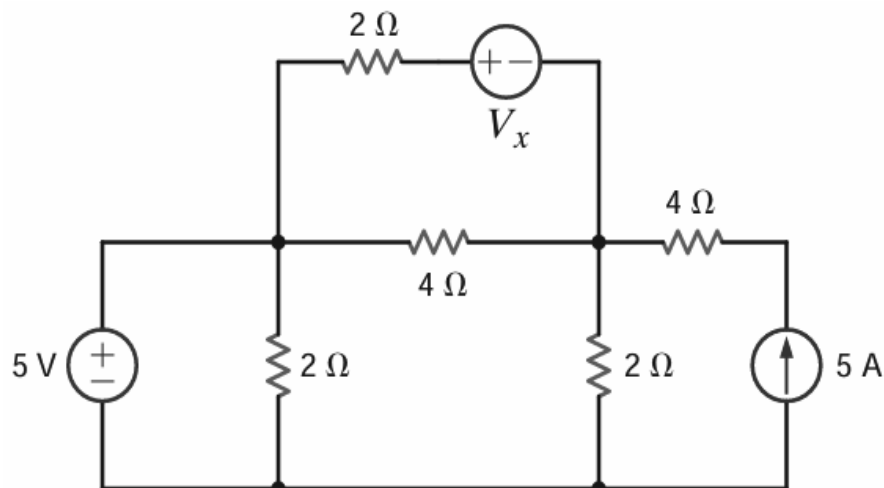
Q5. [10 marks]

Using **nodal analysis**, find the value of V_x , such that the 5-A current source supplies 50 W .




Q6. [10 marks]


Determine all four nodal voltages for the following circuit.

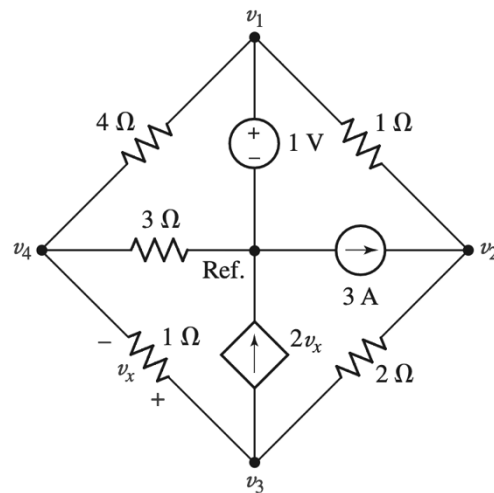**Q7. [10 marks]**

Using **mesh analysis**, determine the power absorbed by the 10-ohm resistor.

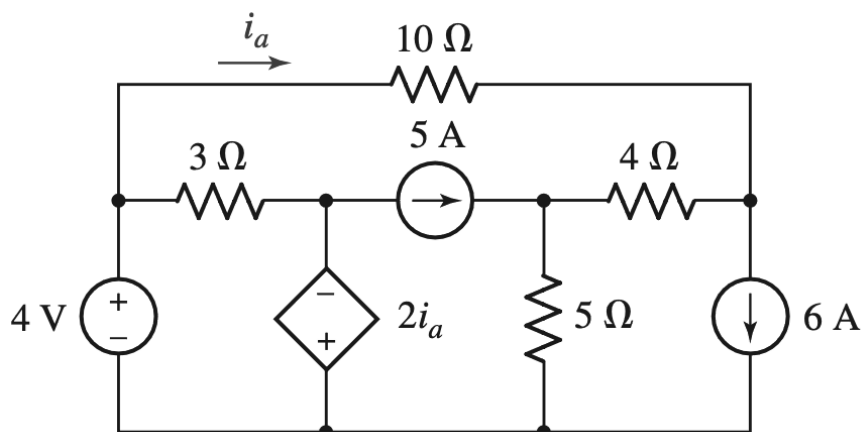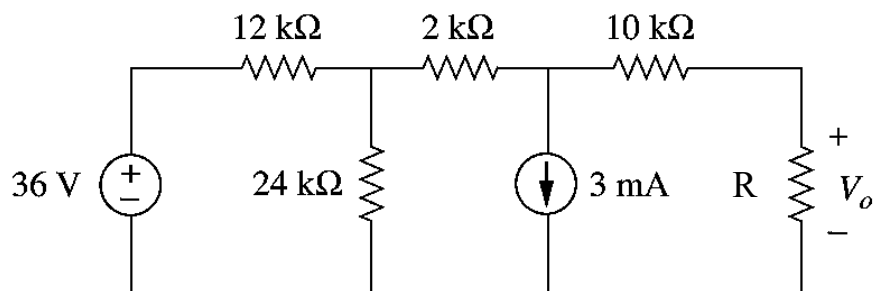
**Q8. [10 marks]**

Using **mesh analysis**, find the value of the resistance, R such that the voltage, $V_0 = -1\text{ V}$, for the following circuit.



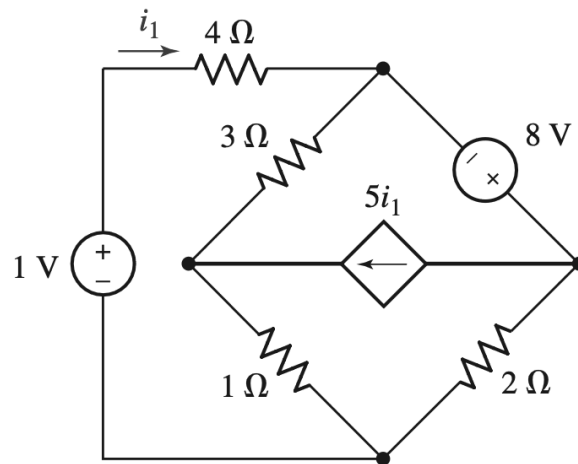
Q9. [10 marks]

Using **mesh analysis**, determine the power supplied by the 1 V source.



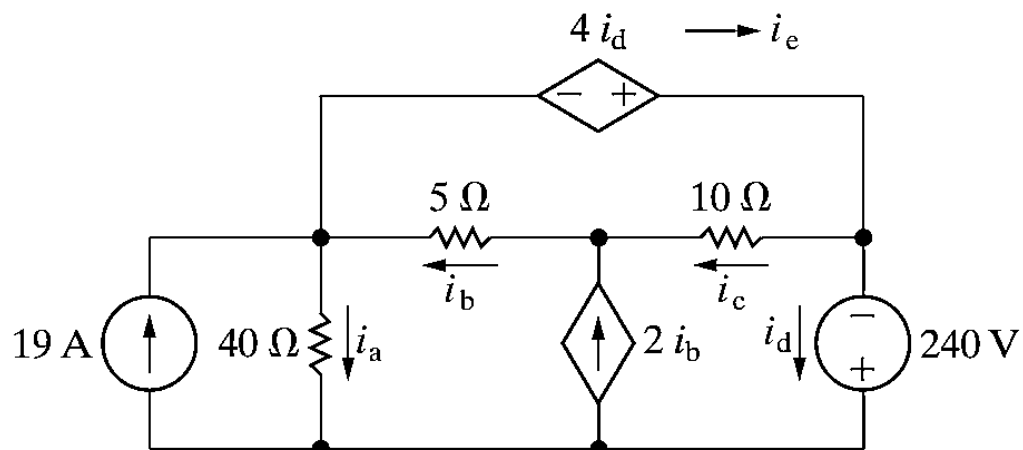
Q10. [10 marks]

Find the branch currents, i_a, i_b, i_c, i_d, i_e for the following circuit using the **mesh analysis technique**.



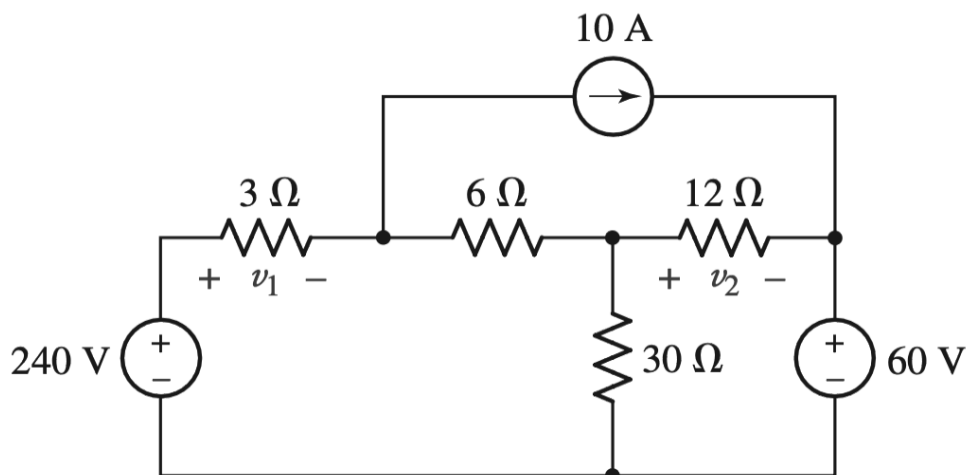
Q11. [10 marks]

Using **mesh analysis**, determine the voltages v_1 and v_2 .



Q12. [10 marks]


For the following circuit, determine i_1 , i_2 , i_3 , and i_4 using mesh analysis.

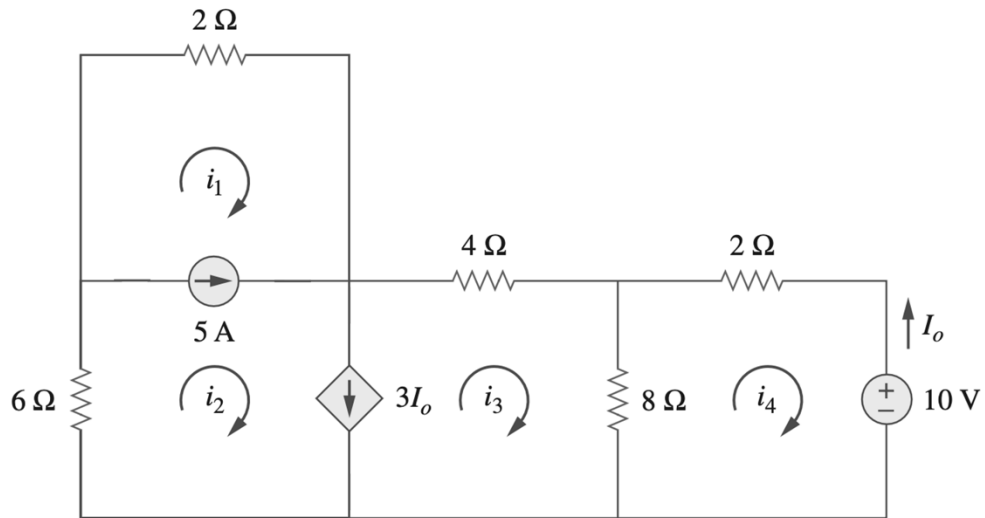

EEE 101
Assignment 1b

Name: Souvik Barman Ratul
ID: 24121205

Ans to the Q. No-1

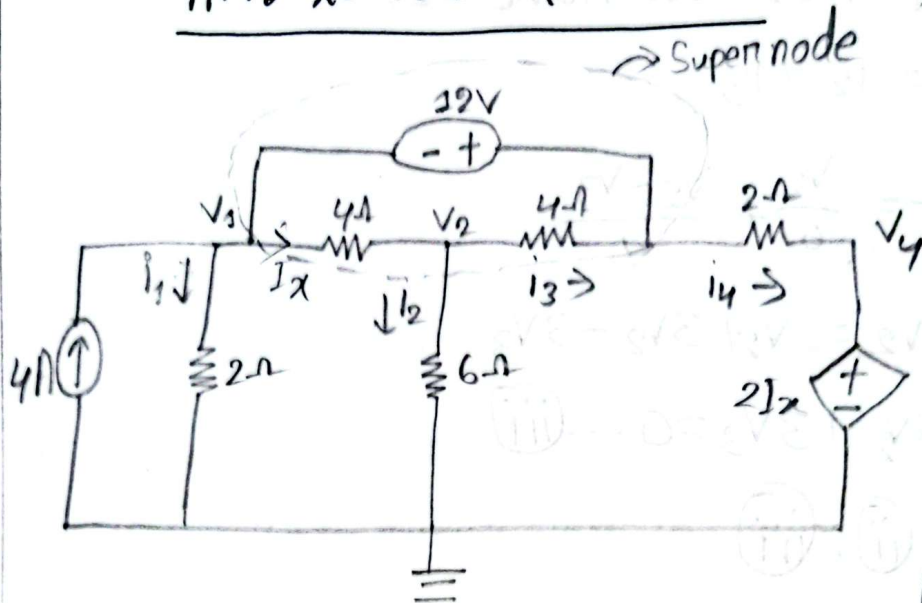

Applying KCL at Supernode,

$$4 + I_3 = I_1 + I_2 + I_4$$

$$\Rightarrow 4 + \frac{V_2 - V_3}{4} = \frac{V_1}{2} + \frac{V_2}{6} + \frac{V_3 - V_4}{2}$$

$$\Rightarrow 3V_1 - 2V_2 + 3V_3 - 2V_4 = 16$$

$$\Rightarrow 3V_1 - 2V_2 + 3V_3 - 2 \times \left(\frac{V_1 - V_2}{2} \right) = 16$$

$$\therefore 2V_1 - V_2 + 3V_3 = 16 \quad \dots \textcircled{i}$$

Applying KVL at Supernode,

$$-V_1 + V_3 - 12 = 0$$

$$\therefore V_3 - V_1 = 12 \quad \dots \textcircled{ii}$$

$$I_1 = \frac{V_1}{2}$$

$$I_2 = \frac{V_2}{6}$$

$$I_3 = \frac{V_2 - V_3}{4}$$

$$I_4 = \frac{V_3 - V_4}{2}$$

$$I_x = \frac{V_1 - V_2}{4}$$

$$\therefore V_4 = 2 I_x$$

$$\Rightarrow V_4 = \frac{V_1 - V_2}{2}$$

Applying KCL at node v_2 ,

$$I_x = i_2 + i_3$$

$$\Rightarrow \frac{V_1 - V_2}{4} = \frac{V_2}{6} + \frac{V_2 - V_3}{4}$$

$$\Rightarrow 3V_1 - 3V_2 = 2V_2 + 3V_2 - 3V_3$$


$$\Rightarrow 3V_1 - 8V_2 + 3V_3 = 0 \dots \textcircled{iii}$$

from $\textcircled{i}$, $\textcircled{ii}$, $\textcircled{iii}$

$$V_1 = -3.65V, V_2 = 1.76V, V_3 = 8.35V$$

$$V_4 = \frac{V_1 - V_2}{2} = \frac{-3.65 - 1.76}{2} = -2.71V \quad \text{Ans}$$

Answer to the Q. No-2

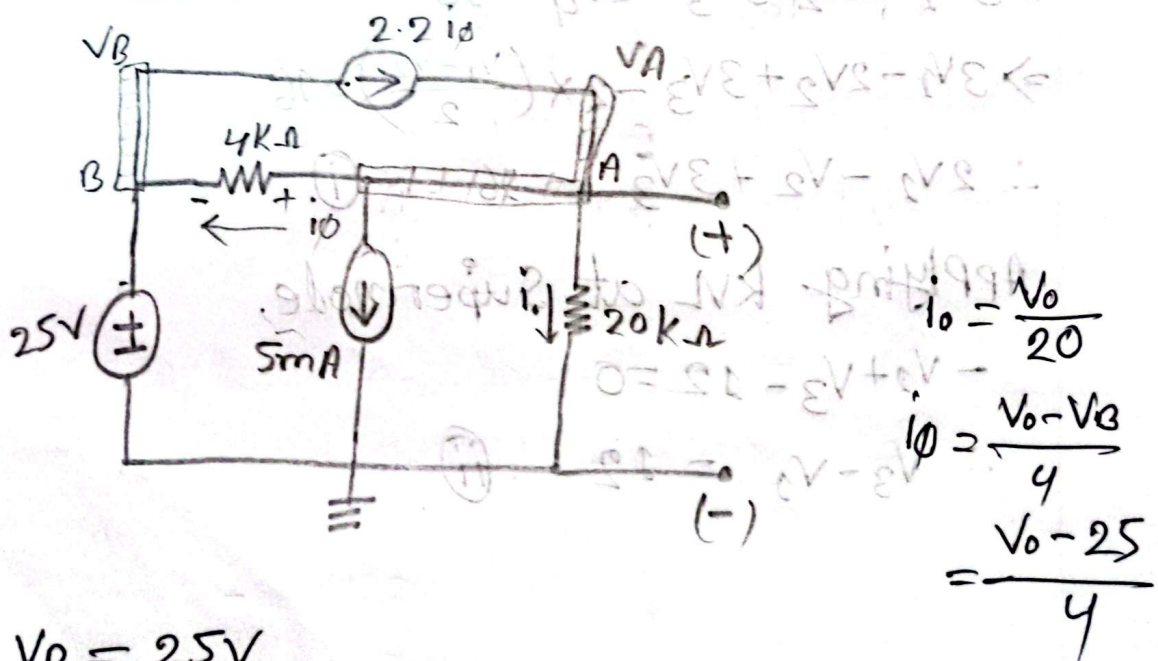

$$V_B = 25V$$

Applying KCL at node A $\Rightarrow$

$$i_0 + i_\phi + 5 = 2 \cdot 2 i_\phi$$

$$\Rightarrow \frac{V_0}{20} + \frac{V_0 - 25}{4} + 5 = 2 \cdot 2 \times \frac{V_0 - 25}{4}$$

$$\Rightarrow \frac{V_0 + 5V_0 - 125 + 100}{20} = \frac{2 \cdot 2V_0 - 55}{4}$$


$$\Rightarrow 24V_0 - 100 = 44V_0 - 1100$$

$$\Rightarrow 44V_0 - 24V_0 = 1100 - 100$$

$$\Rightarrow 20V_0 = 1000$$

$$V_0 = 50V \text{ Ans}$$

Answer to the Q. No-3

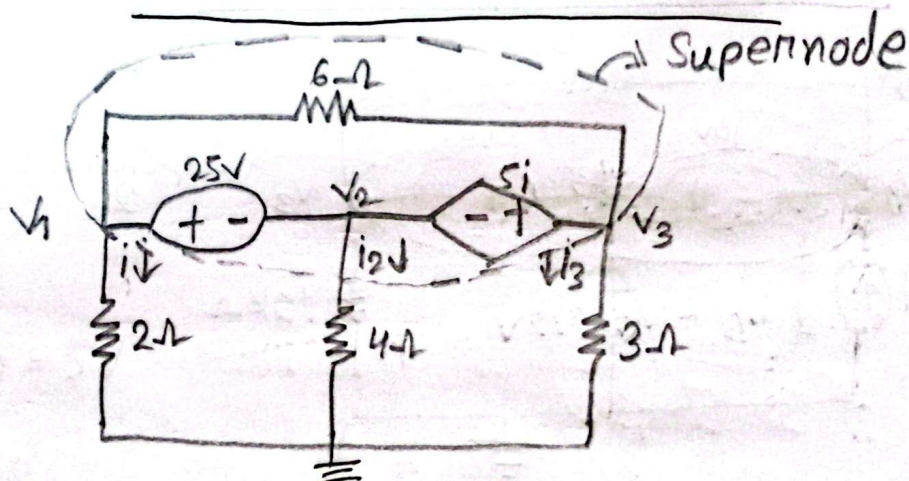

Applying KCL at Supernode,

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0$$

$$\therefore 6V_1 + 3V_2 + 4V_3 = 0 \quad \textcircled{i}$$

again, $V_1 - V_2 = 25 \dots \textcircled{i}$

again, $V_2 - V_3 = -5i$

$\Rightarrow V_2 - V_3 = -\frac{5V_1}{2}$

$\Rightarrow 2V_2 - 2V_3 + 5V_1 = 0 \dots \textcircled{iii}$

From $\textcircled{i}, \textcircled{ii}, \textcircled{iii} \Rightarrow$


$V_1 = 7.61V$

$V_2 = -17.39V$

$V_3 = 1.63V$

Ans

Answer to the Q. NO-4

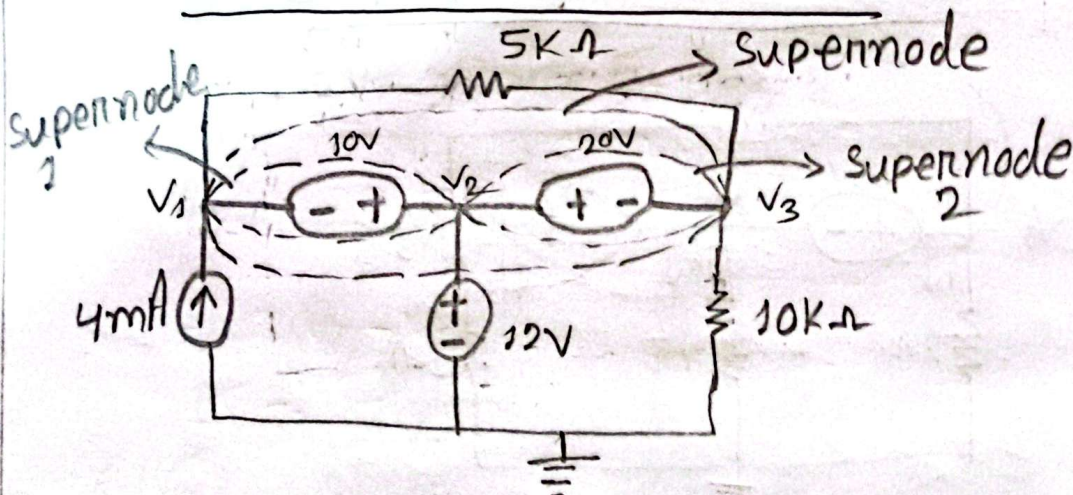

From Supernode-1, $V_2 - V_1 = 10 \dots \textcircled{i}$

From Supernode-2, $V_3 - V_2 = 20 \dots \textcircled{ii}$

again,

$V_2 - 0 = 12$


$V_2 = 12V$

$$\therefore V_1 = 2V$$

$$12 - \sqrt{3} = 20$$

$$\therefore V_3 = -8V$$
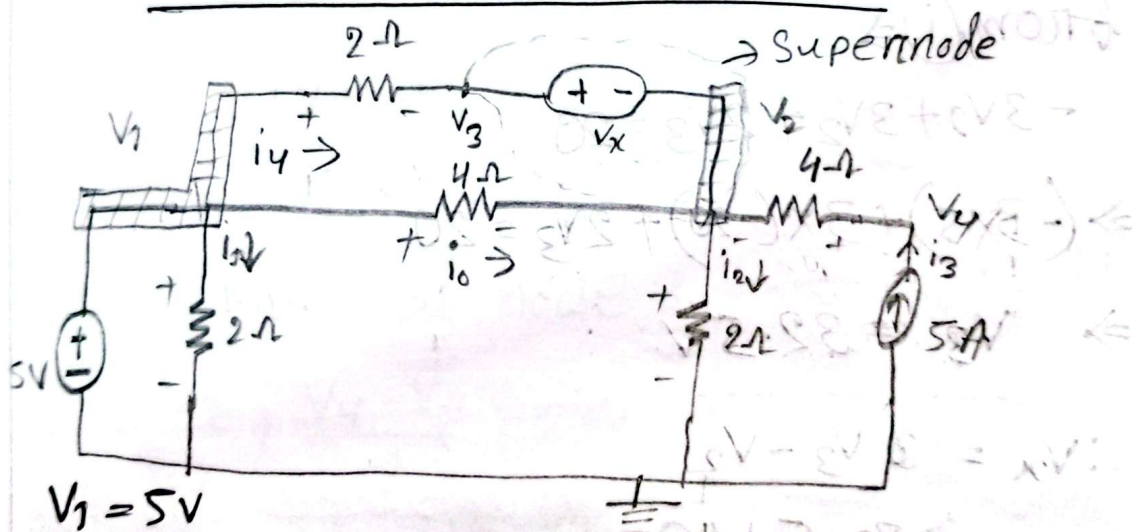
$$\therefore \left. \begin{array}{l} V_1 = 2V \\ V_2 = 12V \\ V_3 = -8V \end{array} \right\} \underline{\text{Ans}}$$



Applying KCL at supernode (v_2, v_x, v_3)

$$i_3 + i_0 = i_2 + i_4$$

$$\Rightarrow 5 + \frac{v_1 - v_2}{4} = \frac{v_2}{2} + \frac{v_3 - v_1}{2}$$

$$\Rightarrow (20 + V_1 - V_2) 2 = (V_2 + V_3 - V_1) \times 4$$

$$\Rightarrow (20 + V_1 - V_2) = (V_2 + V_3 - V_1) \times 2$$

$$\Rightarrow 20 + V_1 - V_2 = 2V_2 + 2V_3 - 2V_1$$

$$\Rightarrow -3V_1 + 3V_2 + 2V_3 = 20 \dots (i)$$

now,

$$P_4 = V_4 I$$

$$\Rightarrow V_4 = \frac{50}{5} = 10V$$

again,

$$V_x = V_3 - V_2$$

$$\left| \frac{V_4 - V_2}{4} = 5 \right.$$

$$\Rightarrow 10 - V_2 = 20$$

$$\Rightarrow V_2 = -10V$$

from (i) $\Rightarrow$

$$-3V_1 + 3V_2 + 2V_3 = 20$$

$$\Rightarrow (-3 \times 5) + 3 \times (-10) + 2V_3 = 20$$

$$\Rightarrow V_3 = 32.5V$$


$$\therefore V_x = V_3 - V_2$$

$$= 32.5 + 10$$

$$= 42.5V$$

Ans

Answer to the Q. No-6

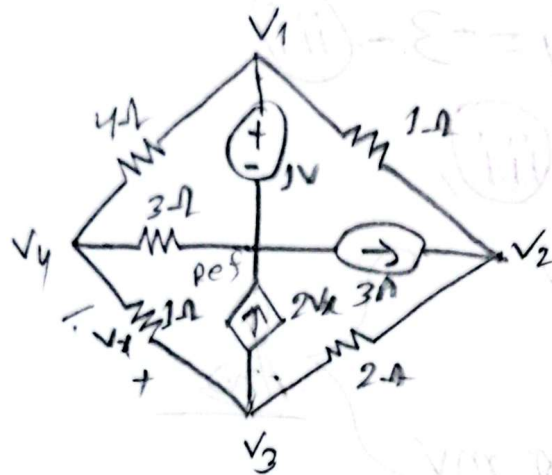

Applying KCL at node-2,

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{2} = 3$$

$$\Rightarrow 2V_2 - 2 + V_2 - V_3 = 6$$

$$\Rightarrow 3V_2 - V_3 = 8 \quad \text{--- (i)}$$

Applying KCL at node-3,

$$\frac{V_2 - V_3}{2} + \frac{V_4 - V_3}{1} = 2V_x$$

$$\Rightarrow 2(V_3 - V_4) = \frac{V_2 - V_3}{2} + V_4 - V_3$$

$$\Rightarrow V_2 - 7V_3 + 6V_4 = 0 \quad \text{--- (ii)}$$

Applying KCL at node-4,

$$\frac{V_4 - V_1}{4} + \frac{V_4}{3} + \frac{V_4 - V_3}{1} = 0$$

$$\Rightarrow 3V_4 - 3V_3 + 4V_4 + 12V_4 - 12V_3 = 0$$

$$\Rightarrow 12V_3 - 19V_4 = -3 \quad \text{--- (ii)}$$

from (i), (ii), (iii),


$$V_2 = 3.085 \text{ V}$$

$$V_3 = 2.256 \text{ V}$$

$$V_4 = 951.219 \text{ mV}$$

Ans

Answer to the Q. No-7

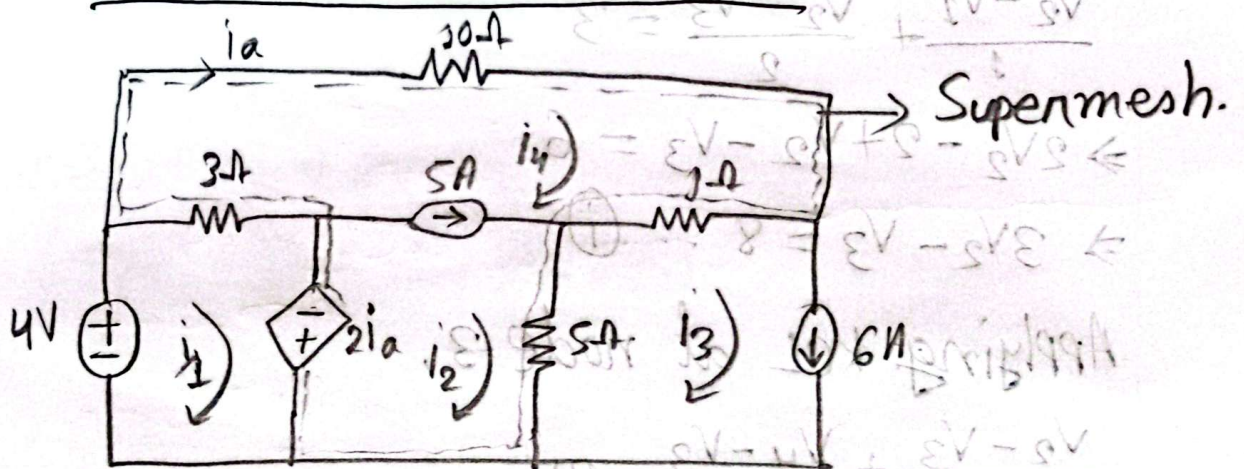

Applying ~~KVL~~ KVL on ~~meshes~~ Supermesh,

$$10i_4 + 4(i_4 - i_3) + 5(i_2 - i_3) + 2i_a + 3(i_4 - i_3) = 0$$

$$\Rightarrow 10i_4 + 4i_4 - 4i_3 + 5i_2 - 5i_3 + 2i_4 + 3i_4 - 3i_3 = 0 \quad [i_4 = i_a]$$

$$\therefore -3i_3 + 5i_2 + 19i_4 = 54 \quad \text{--- (i)}$$

Applying KCL on Supermesh,

$$i_2 - i_4 = 5 \dots \textcircled{ii}$$

Applying KVL on mesh-1,

$$3(i_2 - i_4) - 2i_1 - 4 = 0$$

$$\Rightarrow 3i_1 - 3i_4 - 2i_1 - 4 = 0 \quad [i_1 = i_4]$$

$$\therefore 3i_1 - 5i_4 = 4 \dots \textcircled{iii}$$

Applying KVL on mesh-4,

$$i_4 = -5A.$$

From, $\textcircled{i}$, $\textcircled{ii}$, $\textcircled{iii} \Rightarrow$

$$i_1 = 4.23A$$

$$i_2 = 6.74A$$


$$i_4 = 1.74A.$$

$$\therefore i_x = i_4 = 1.74A.$$

$$\begin{aligned} \downarrow \text{Power absorbed by } 10\Omega \text{ resistor, } p &= i_x^2 \times 10 \\ &= (1.74)^2 \times 10 \\ &= 30.1662 \text{ W} \end{aligned}$$

Ans

Answer to the q. No-8

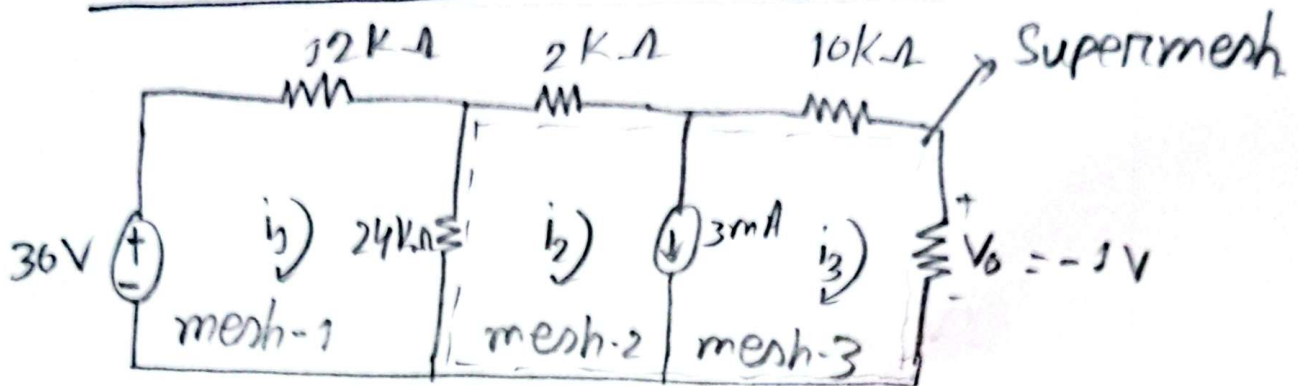

Applying KVL on Supermesh,

$$24(i_2 - i_1) + 2i_2 + 10i_3 - 1 = 0$$

$$\Rightarrow -24i_1 + 26i_2 + 10i_3 = 1 \quad \text{--- (i)}$$

Applying KCL on Supermesh,

$$i_2 - i_3 = 3 \quad \text{--- (ii)}$$

Applying KVL on mesh-1,

$$12i_1 + 24(i_1 - i_2) - 36 = 0$$


$$\Rightarrow 36i_1 - 24i_2 = 36 \quad \text{--- (iii)}$$

from (i), (ii), (iii) $\rightarrow$

$$i_1 = 2.83 \text{ A}, \quad i_2 = 2.75 \text{ A}, \quad i_3 = -0.25 \text{ A}$$

$$R = \frac{V_o}{i_3} = \frac{-1}{-0.25} = 4 \text{ k}\Omega \quad \underline{\text{Ans}}$$

Answer to the Q. No-9

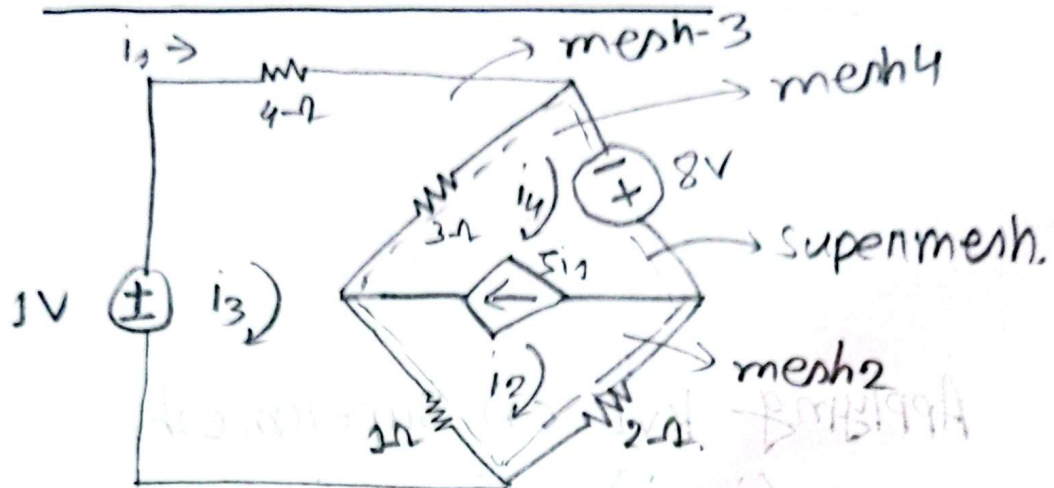

Applying KVL on super mesh,

$$3(i_4 - i_3) - 8 + 2i_2 + 1(i_2 - i_3) = 0$$

$$\Rightarrow 3i_4 + 3i_2 - 4i_3 = 8 \quad \text{--- (i)}$$

Applying KCL on super mesh,

$$i_4 - i_2 = 5i_1$$

$$\Rightarrow i_4 - i_2 = 5i_3 \quad [i_1 = i_3]$$

$$\therefore i_4 - i_2 = 5i_3 = 0 \quad \text{--- (ii)}$$

Applying KVL on mesh 3,

$$-1 + 4i_3 + 3(i_3 - i_4) + 1(i_3 - i_2) = 0$$

$$\Rightarrow -3i_4 - i_2 + 8i_3 = 1 \quad \text{--- (iii)}$$

from, (i), (ii), (iii)

$$i_2 = -33.5 \text{ A}$$


$$i_3 = 19 \text{ A}$$

$$i_4 = 61.5 \text{ A}$$

The power supplied by the 1V source is

$$\begin{aligned} P &= V i_3 \\ &= 1 \times 19 \\ &= 19 \text{ W} \text{ Ans} \end{aligned}$$

Ans to the Q. No - 10

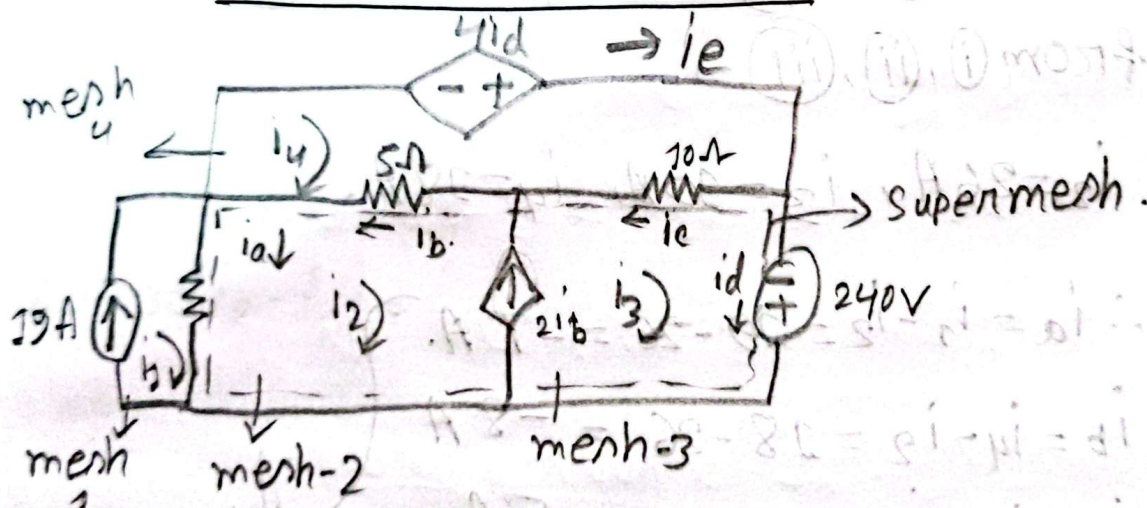

Applying KVL on Supermesh,

$$40(i_2 - i_3) + 5(i_2 - i_4) + 10(i_3 - i_4) - 240 = 0$$

$$\Rightarrow -40i_2 + 45i_2 + 10i_3 - 15i_4 = 240$$

$$\Rightarrow 45i_2 + 10i_3 - 15i_4 = 1000 \dots (i) \quad [i_1 = 19 \text{ A}]$$

Applying KCL on Supermesh,

$$i_3 - i_2 = 2i_b$$

$$\Rightarrow i_3 - i_2 = 2(i_4 - i_2) \quad [i_b = i_4 - i_2]$$

$$\Rightarrow -i_2 - i_3 + 2i_4 = 0 \dots (ii)$$

Applying KVL on mesh-4,

$$-4i_a + 10(i_4 - i_3) + 5(i_4 - i_2) = 0$$

$$\Rightarrow -4i_3 + 10i_4 - 10i_3 + 5i_4 - 5i_2 = 0, \quad [i_d = i_3]$$

$$\Rightarrow -5i_2 - 14i_3 + 15i_4 = 0 \dots (iii)$$

from (i), (ii), (iii) $\Rightarrow$

$$i_2 = 26A, \quad i_3 = 10A, \quad i_4 = 18A.$$

$$\therefore i_a = i_1 - i_2 = 19 - 26 = -7A.$$

$$i_b = i_4 - i_2 = 18 - 26 = -8A$$


$$i_c = i_4 - i_3 = 18 - 10 = 8A$$

$$i_d = i_3 = 10A$$

$$i_e = i_4 = 18A$$

Ans

Ans to the Q. NO-11

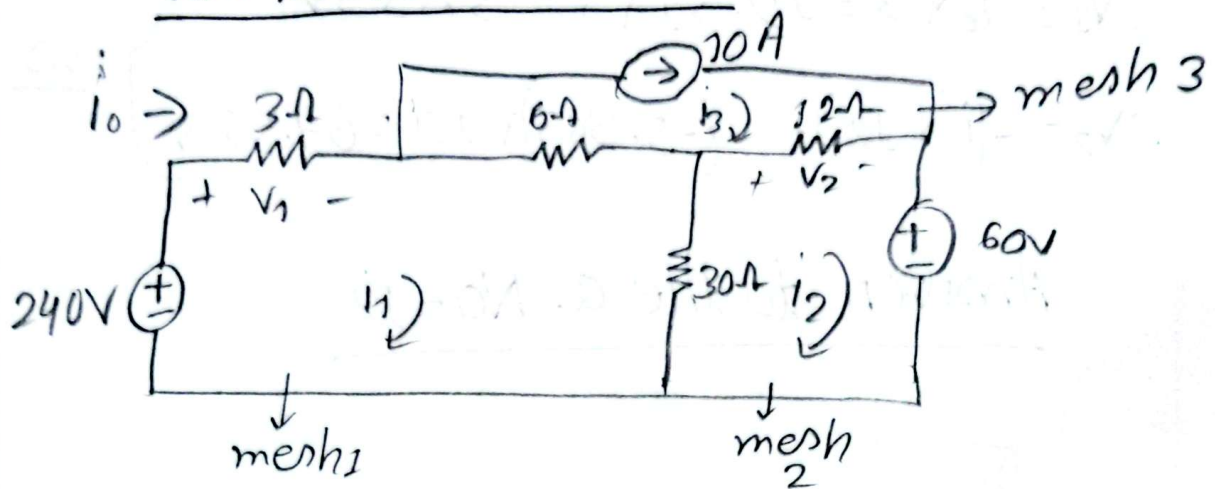

Applying KVL on mesh 1,

$$-240 + 3i_1 + 6(i_1 - i_3) + 30(i_1 - i_2) = 0$$

$$\Rightarrow -240 + 3i_1 + 6i_1 - (6 \times 10) + 30i_1 - 30i_2 = 0$$

$$\Rightarrow 39i_1 - 30i_2 = 300 \quad \text{--- (i)}$$

Applying KVL on mesh-2

$$60 + 30(i_2 - i_1) + i_2(i_2 - i_3) = 0$$

$$\Rightarrow 60 + 30i_2 - 30i_1 + 12i_2 - 12 \times 10 = 0$$

$$\Rightarrow 42i_2 - 30i_1 = 6 \quad \text{--- (ii)}$$


From,

$$i_1 = 19.5 \text{ A}, \quad i_2 = 15.365 \text{ A}$$

$$i_0 = i_1 = 19.5 \text{ A}, \quad i' = i_3 - i_2 = (10 - 15.365) \text{ A} \\ = -5.365 \text{ A}$$

$$\begin{aligned} \therefore V_1 &= I_0 \times 3 = 19.51 \times 3 = 58.53 \text{ V} \\ \therefore V_2 &= -(i' \times 12) = -(-5.365) \times 12 = 64.38 \text{ V} \end{aligned} \quad \left. \vphantom{\begin{aligned} \therefore V_1 &= I_0 \times 3 = 19.51 \times 3 = 58.53 \text{ V} \\ \therefore V_2 &= -(i' \times 12) = -(-5.365) \times 12 = 64.38 \text{ V} \end{aligned}} \right\} \underline{\text{Ans}}$$

Answer to the q. No-12

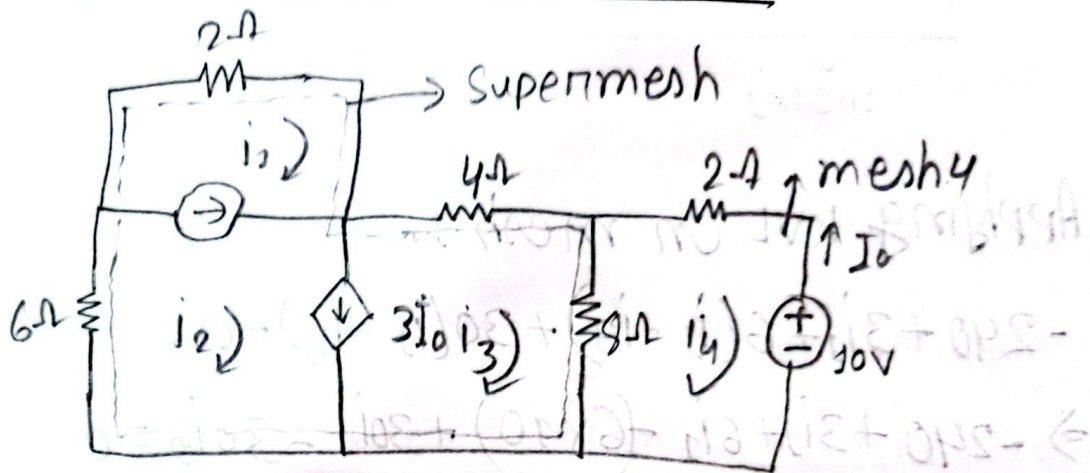

Applying KVL around Supermesh,

$$\begin{aligned} 6i_2 + 2i_1 + 4i_3 + 8(i_3 - i_4) &= 0 \\ \Rightarrow i_1 + 3i_2 + 6i_3 - 4i_4 &= 0 \quad \text{--- (i)} \end{aligned}$$

Applying KVL around mesh-4,

$$\begin{aligned} 8(i_4 - i_3) + 2i_4 + 10 &= 0 \\ \Rightarrow 5i_4 - 4i_3 &= -5 \quad \text{--- (ii)} \end{aligned}$$

Applying KCL on Supermesh,

$$i_2 - i_3 = 3I_0$$

$$\Rightarrow i_2 - i_3 = -3i_4 \quad [I_0 = -i_4]$$

$$\Rightarrow i_2 - i_3 + 3i_4 = 0 \dots \textcircled{iii}$$

Applying KCL,

$$i_2 - i_1 = 5 \dots \textcircled{iv}$$

From, $\textcircled{i}, \textcircled{ii}, \textcircled{iii}, \textcircled{iv}$

$$i_1 = -7.5A, i_2 = -2.5A, i_3 = 3.93A, i_4 = 2.143A$$

Ans